

Digital Logic Systems

Recitation 12: Foundations of Synchronous Circuits & Synchronous Modules

Guy Even Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

January 17, 2012

The Canonic Form of a Synchronous Circuit

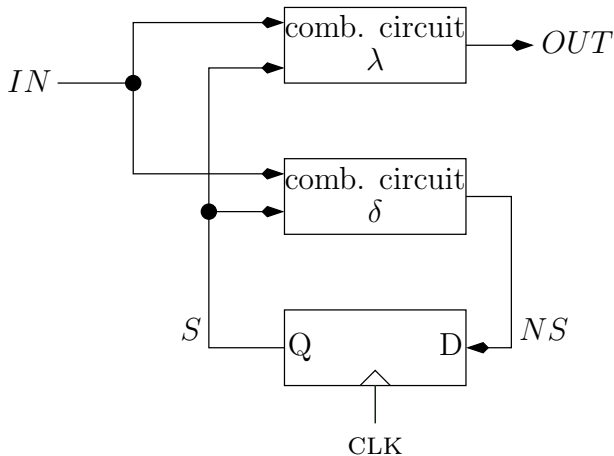


Figure: A synchronous circuit in canonic form.

Definition

A *finite state machine* (FSM) is a 6-tuple $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$, where

- Q is a set of *states*.
- Σ is the alphabet of the input.
- Δ is the alphabet of the output.
- $\delta : Q \times \Sigma \rightarrow Q$ is a *transition function*.
- $\lambda : Q \times \Sigma \rightarrow \Delta$ is an *output function*.
- $q_0 \in Q$ is an *initial state*.

Algorithm $\text{Min-}\Phi(C)$

The input of algorithm $\text{Min-}\Phi(C)$ consists of:

- 1 A description of the circuit C , namely, a directed graph $G = (V, E)$ and a labeling $\pi : V \rightarrow \Gamma \cup IO \cup \{FF\}$,
- 2 $pd(IN)$ for every input signal IN , and
- 3 $setup(OUT)$ for every output signal OUT .

Algorithm 1 $\text{Min-}\Phi(C)$ - an algorithm that computes the minimum clock period of a synchronous circuit C .

- ① Let C' denote the combinational circuit obtained from C by stripping away the flip-flops.
- ② Assign delays $d(v)$ to vertices in C' as follows.

$$d(v) \triangleq \begin{cases} pd(IN) & \text{if input gate } v \text{ feeds } IN. \\ t_{pd}(FF) & \text{if } v \text{ corresponds to } Q\text{-port of a flip-flop.} \\ setup(OUT) & \text{if output gate } v \text{ is fed by } OUT. \\ t_{su}(FF) & \text{if } v \text{ corresponds to } D\text{-port of a flip-flop.} \\ pd(\pi(v)) & \text{if } \pi(v) \text{ is a combinational gate.} \end{cases}$$

- ③ Compute

$$\Phi^* \triangleq \max\{d(p) \mid p \text{ is a path from a source to a sink in } C'\}.$$

- ④ Return(Φ^*).

The zero delay model

In the zero delay model **transitions** of all signals are **instantaneous**. This means that the propagation delay and contamination delay of combinational circuits is zero. In addition, the parameters of flip-flops satisfy:

$$\begin{aligned}t_{su} &= t_{i+1} - t_i, \\t_{hold} &= t_{cont} = t_{pd} = 0.\end{aligned}$$

We emphasize that this model is used only as a simplified model for specifying and simulating the functionality of circuits with flip-flops.

Zero delay model - cont

For simplicity, we normalize time so that the clock period is 1 time unit. That is, $t_{i+1} - t_i = 1$, for every i . This allows us to specify the functionality of a flip-flop in the zero delay model as follows:

$$Q(t + 1) = D(t).$$

The meaning of this specification is as follows. (1) The critical segment C_i equals $[t_{i-1}, t_i)$. (2) The value of $D(t)$ is stable during the critical segment $[t_{i-1}, t_i)$. This value is sampled by the flip-flop during the clock cycle $(i - 1)$. In the next clock cycle $[t_i, t_{i+1})$, the flip-flop's output $Q(t)$ equals the value of the input sampled during the previous cycle.

We assume that the flip-flops are initialized. Formally, let F denote the set of flip-flops in the synchronous circuit. Let $S_0 : F \rightarrow \{0, 1\}$ denote a function that specifies the initial values of each flip-flop. Let I denote the set of input gates in the synchronous circuit. Let $IN_i : I \rightarrow \{0, 1\}$ denote a function that specifies the input fed by each input gate in clock cycle i .

Algorithm 2 $\text{SIM}(C, S_0, \{IN_i\}_{i=0}^{n-1})$ - An algorithm for simulating a synchronous circuit C with respect to an initialization S_0 and a sequence of inputs $\{IN_i\}_{i=0}^{n-1}$.

- ① Construct the combinational circuit C' obtained from C by stripping away the flip-flops.
 - ② For $i = 0$ to $n - 1$ do:
 - ① Simulate the combinational circuit C' with input values corresponding to S_i and IN_i . Namely, every input gate in C feeds a value according to IN_i , and every Q -port of a flip-flop feeds a value according to S_i . For every sink z in C' , let z_i denote the value fed to z according to this simulation.
 - ② For every Q -port S of a flip-flop, define $S_{i+1} \leftarrow NS_i$, where NS denotes the D -port of the flip-flop.
-

Two tasks are often associated with synchronous circuits. These tasks are defined as follows.

- 1 Analysis: given a synchronous circuit C , describe its functionality by an FSM.
- 2 Synthesis: given an FSM \mathcal{A} , design a synchronous circuit C that implements \mathcal{A} .

The task of analyzing a synchronous circuit C is carried out as follows.

- ① Define the FSM $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$ as follows.
 - ① The set of **states** is $Q \triangleq \{0, 1\}^k$, where k denotes the number of flip-flops in C .
 - ② Define the **initial state** q_0 to be the initial outputs of the flip-flops.
 - ③ $\Sigma = \{0, 1\}^\ell$, where ℓ denotes the number of **input** gates in C .
 - ④ $\Delta = \{0, 1\}^r$, where r denotes the number of **output** gates in C .
 - ⑤ **Transform** C to a functionally equivalent synchronous circuit \tilde{C} in **canonic form**. Compute the truth tables of the combinational circuits λ and δ . Define the **Boolean functions** according to these **truth tables**.

Given an FSM $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$, the task of designing a synchronous circuit C that implements \mathcal{A} is carried out as follows.

- 1 Encode Q, Σ and Δ by binary strings. Formally, let f, g, h denote one-to-one functions, where

$$f : Q \rightarrow \{0, 1\}^k$$

$$g : \Sigma \rightarrow \{0, 1\}^\ell$$

$$h : \Delta \rightarrow \{0, 1\}^r.$$

- 2 Design a combinational circuit C_δ that implements the (partial) Boolean function $B_\delta : \{0, 1\}^k \times \{0, 1\}^\ell \rightarrow \{0, 1\}^k$ defined by

$$B_\delta(f(x), g(y)) \triangleq f(\delta(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

- 3 Design a combinational circuit C_λ that implements the (partial) Boolean function $B_\lambda : \{0,1\}^k \times \{0,1\}^\ell \rightarrow \{0,1\}^r$ defined by

$$B_\lambda(f(x), g(z)) \triangleq f(\lambda(x, z)), \text{ for every } (x, z) \in Q \times \Sigma.$$

- 4 Let C denote the synchronous circuit in canonic form constructed from k flip-flops and the combinational circuits C_δ for the next state and C_λ for the output.

Let C denote the synchronous circuit in canonic form constructed from k flip-flops and the combinational circuits C_δ for the next state and C_λ for the output.

The description of the encoding step leaves a great deal of freedom. Since $|\{0,1\}^k| \geq |Q|$, it follows that $k \geq \log_2 |Q|$, and similar bounds apply to ℓ and r . However, it is not clear that using the smallest lengths is the best idea. Certain encodings lead to more complicated Boolean functions B_δ and B_λ . Thus, the question of selecting a “good” encoding is a very complicated task, and there is no simple solution to this problem.

Example: A two-state FSM

Consider the FSM $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$ depicted in the next figure, where

$$Q = \{q_0, q_1\},$$

$$\Sigma = \Delta = \{0, 1\}.$$

 


Figure: A two-state FSM.

Two-State FSMs: Synthesis

Given an FSM $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$, the synchronous circuit C that is obtained by executing the synthesis procedure is as follows. We encode Q, Σ and Δ by binary strings. Formally, let f, g, h denote one-to-one functions, where

$$f : Q \rightarrow \{0, 1\}$$

$$g : \Sigma \rightarrow \Sigma$$

$$h : \Delta \rightarrow \Delta,$$

where

$$f(q_0) = 0, f(q_1) = 1,$$

and

$$\forall x \in \{0, 1\} : g(x) = h(x) = x.$$

Two-State FSMs: Synthesis - C_δ

We design a combinational circuit C_δ that implements the Boolean function $B_\delta : \{0, 1\}^2 \rightarrow \{0, 1\}$ defined by

$$B_\delta(f(x), g(y)) \triangleq f(\delta(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

$f(x)$	$g(y)$	$f(\delta(x, y))$
0	0	1
1	0	1
0	1	0
1	1	0

Table: The truth table of B_δ .

It follows that $B_\delta(f(x), g(y)) = \text{NOT}(g(y))$.

Two-State FSMs: Synthesis - C_λ

We design a combinational circuit C_λ that implements the Boolean function $B_\lambda : \{0, 1\}^2 \rightarrow \{0, 1\}$ defined by

$$B_\lambda(f(x), g(y)) \triangleq h(\lambda(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

$f(x)$	$g(y)$	$h(\lambda(x, y))$
0	0	1
1	0	1
0	1	0
1	1	1

Table: The truth table of B_λ .

It follows that $B_\lambda(f(x), g(y)) = f(x) \vee \overline{g(y)}$.

Two-State FSMs: Synthesis - the Synch. circuit C

The synchronous circuit in canonic form constructed from a flip-flops and three combinational circuits is depicted in Figure 3.

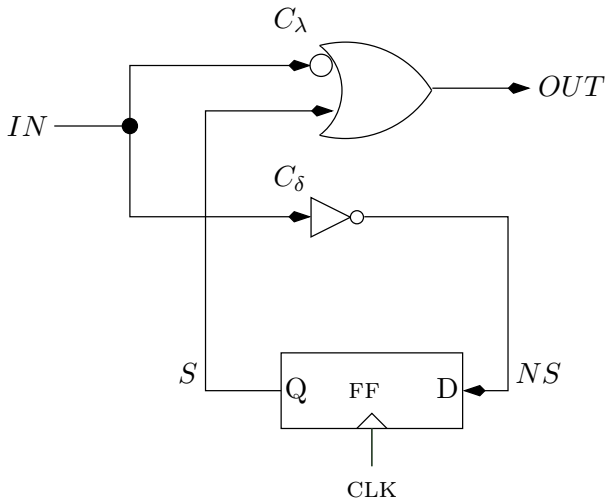


Figure: The output of the synthesis procedure on A .

Sequential Adder

Definition

A *sequential adder* is defined as follows.

Inputs: A, B, reset and a clock signal CLK , where $A_i, B_i, \text{reset}_i \in \{0, 1\}$.

Output: S , where $S_i \in \{0, 1\}$.

Functionality: The *reset* signal is an initialization signal that satisfies:

$$\text{reset}_i = \begin{cases} 1 & \text{if } i = 0, \\ 0 & \text{if } i > 0. \end{cases}$$

Then, for every $i \geq 0$,

$$\langle A[i : 0] \rangle + \langle B[i : 0] \rangle = \langle S[i : 0] \rangle \pmod{2^{i+1}}.$$

Sequential Adder (cont.)

What happens if the value of the input *reset* equals 1 in more than once cycle? The above definition means that if $reset_i = 1$, then we forget about the past, we treat clock cycle (t_i, t_{i+1}) as the first clock cycle.

Formally, we define the last initialization $r(i)$ as follows:

$$r(i) \triangleq \max\{j \leq i : reset_j = 1\}.$$

Namely, $r(i)$ specifies the **last** time $reset_j = 1$ not after cycle i . If $reset_j = 0$, for every $j \leq i$, then $r(i)$ is not defined, and functionality is unspecified. If $r(i)$ is well defined, then the specification is that, for every $i \geq 0$,

$$\langle A[i : r(i)] \rangle + \langle B[i : r(i)] \rangle = \langle S[i : r(i)] \rangle \pmod{2^{i+1}}.$$

Sequential Adder: Implementation

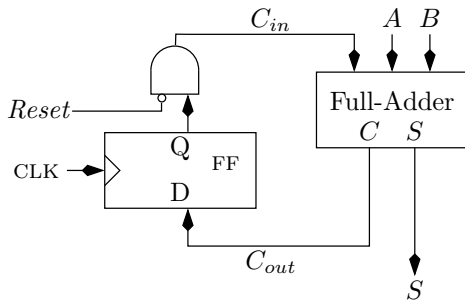


Figure: A synchronous circuit that implements a sequential adder.

Sequential Adder: Implementation - correctness

Theorem

$$\sum_{j=0}^i A_j \cdot 2^j + \sum_{j=0}^i B_j \cdot 2^j = \sum_{j=0}^i S_j \cdot 2^j + c_{out}(i) \cdot 2^{i+1} .$$

Proof.

The proof is by induction on i . The induction basis for $i = 0$ follows from the functionality of the full-adder:

$$A_0 + B_0 + C_{in}(0) = 2 \cdot C_{out}(0) + S_0 .$$



Sequential Adder: Implementation - correctness (cont.)

Proof.

We now prove the induction step for $i > 0$.

$$\begin{aligned}\sum_{j=0}^i A_j \cdot 2^j + \sum_{j=0}^i B_j \cdot 2^j &= (A_i + B_i) \cdot 2^i + \sum_{j=0}^{i-1} A_j \cdot 2^j + \sum_{j=0}^{i-1} B_j \cdot 2^j \\&= (A_i + B_i) \cdot 2^i + \sum_{j=0}^{i-1} S_j \cdot 2^j + C_{out}(i-1) \cdot 2^i \\&= (C_{in}(i) + A_i + B_i) \cdot 2^i + \sum_{j=0}^{i-1} S_j \cdot 2^j \\&= (S_i + 2 \cdot C_{out}(i)) \cdot 2^i + \sum_{j=0}^{i-1} S_j \cdot 2^j \\&= \sum_{j=0}^i S_j \cdot 2^j + C_{out}(i) \cdot 2^{i+1}.\end{aligned}$$

Sequential Adder: Analysis

 


Figure: an FSM of a sequential adder (each transition is labeled by a pair: the condition that the input satisfies and the value of the output).

Sequential Adder: Executing $\text{Min-}\Phi(C)$.

Let C denote the Sequential Adder that we have just implemented.

Assume that all the parameters equal to '1'. Assume that a full adder is implemented by a single gate.

Execute the $\text{Min-}\Phi(C)$ algorithm. **Note** that the *reset* signal is also an input signal, hence we should assign a weight to the input gate that feeds it as well.

The “heaviest” path is of weight 5 (*reset* input gate \rightarrow NOT gate \rightarrow AND gate \rightarrow Full adder gate \rightarrow the output gate the corresponds to the D port), hence $\varphi^* = 5$.