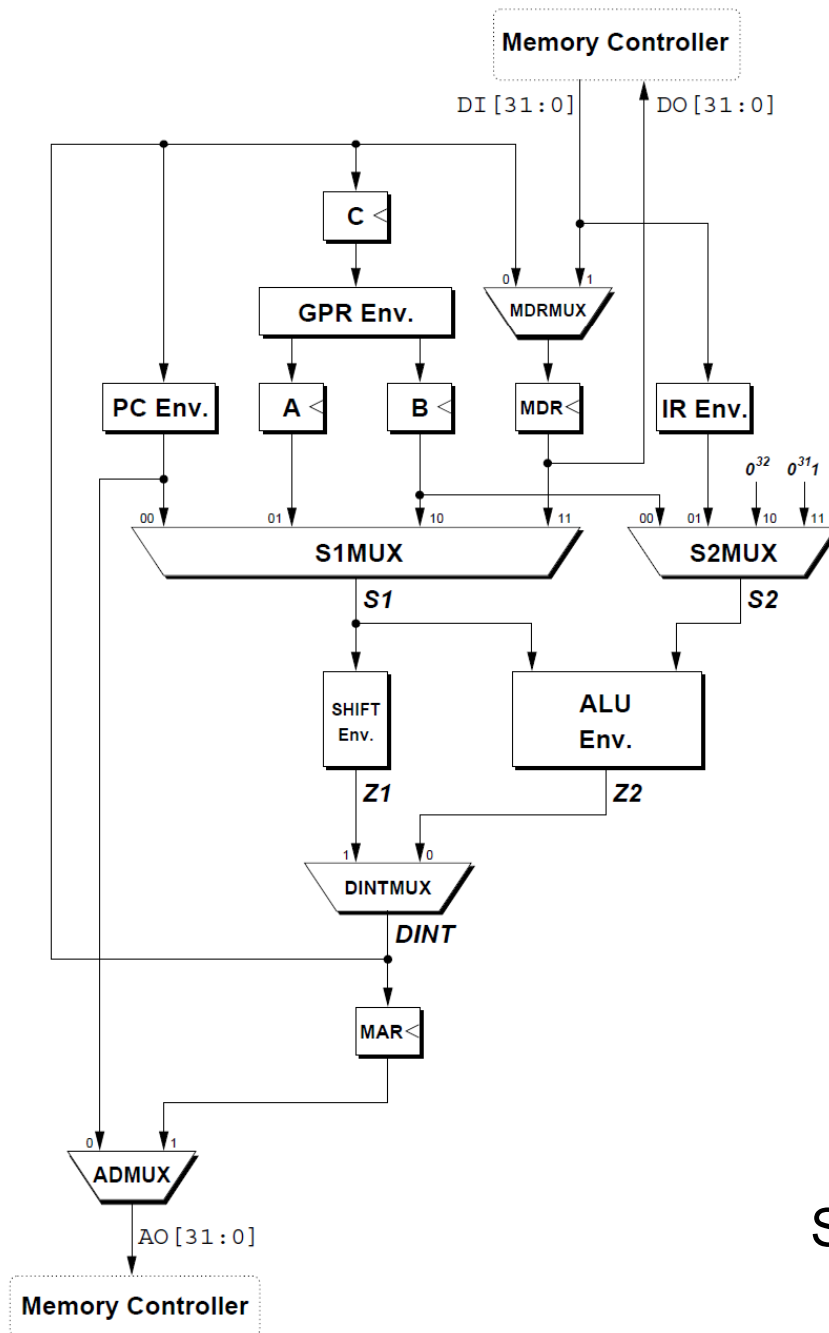


A Simplified DLX: Implementation






Guy Even and Moti Medina

School of Electrical Engineering Tel-Aviv Univ.


January 30, 2012

Name	RTL Instruction	Active Control Outputs	Signal	Value	Semantics	condition	when does it equal 1?
Fetch	$IR = M[PC]$	MR, IRce	ALUF[2:0]		Controls the functionality of ALU	D1	special NOP
Decode	$A = RS1$ $B = RS2$ $PC = PC + 1$	Ace, Bce, S2sel[1], S2sel[0], add, PCce	Rce		Register clock enable	D2	beqz, bnez
Alu	$C = A \text{ op } B$	S1sel[0], Cce, active bits in ALUF[2:0]	S1sel[1:0]	00 01 10 11	PC A B MDR	D3	jalr
TestI	$C = (A \text{ rel } imm)$	S1sel[0], S2sel[0], Cce, test, Itype, active bits in ALUF[2:0]	S2sel[1:0]	00 01 10 11	B IR 0 1	D4	jr
AluI(add)	$C = A + imm$	S1sel[0], S2sel[0], Cce, add, Itype	DINTsel	0 1	ALU Shifter	D5	lw, sw
Shift	$C = A \text{ shift } sa$ $sa = 1, (-1)$	S1sel[0], Cce DINTsel, shift (.right)	MDRsel	0 1	DINT DI	D6	sgti, seqi, sgei, slti, snei, slei
Adr.Comp	$MAR = A + imm$	S1sel[0], S2sel[0], MARce, add	ADsel	0 1	PC MAR	D7	addi
Load	$MDR = M[MAR]$	MDRce, ADsel, MR, MDRsel	shift		explicit Shift-Instruction	D8	sll, srl
Store	$M[MAR] = MDR$	ADsel, MW	right		Shift to the right	D9	add, sub, and, or, xor
CopyMDR2C	$C = MDR(\gg 0)$	S1sel[0], S1sel[1], S2sel[1], DINTsel, Cce	add		Forces an addition	D10	halt
CopyGPR2MDR	$MDR = B(\ll 0)$	S1sel[1], S2sel[1], DINTsel, MDRce	test		Forces a test (in the ALU)		
WBR	$RD = C$ (R-type)	GPR_WE	MR		Memory Read		
WBI	$RD = C$ (I-type)	GPR_WE, Itype	MW		Memory Write		
Branch	branch taken?		GPR_WE		GPR write enable		
Btaken	$PC = PC + imm$	S2sel[0], add, PCce	itype		Itype-Instruction		
JR	$PC = A$	S1sel[0], S2sel[1], add, PCce	jlink		jump and link		
Save PC	$C = PC$	S2sel[1], add, Cce					
JALR	$PC = A$ $R31 = C$	S1sel[0], S2sel[1], add, PCce, GPR_WE, jlink					

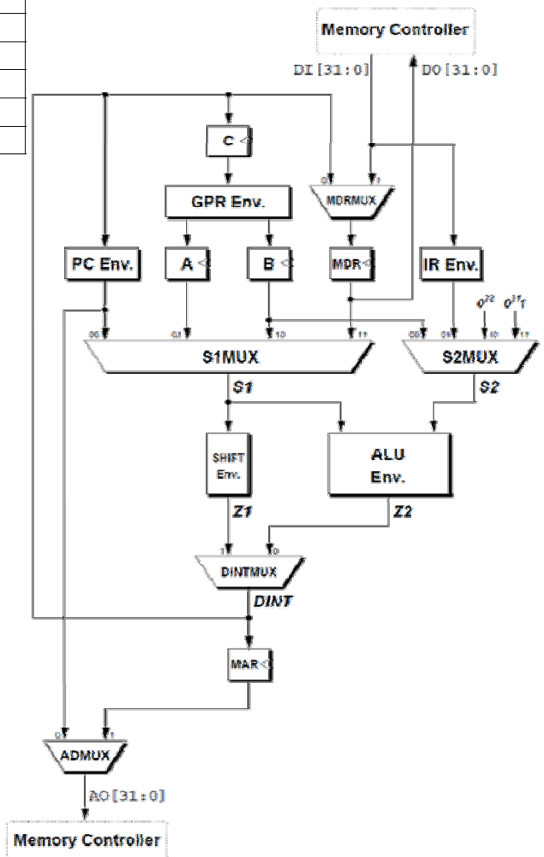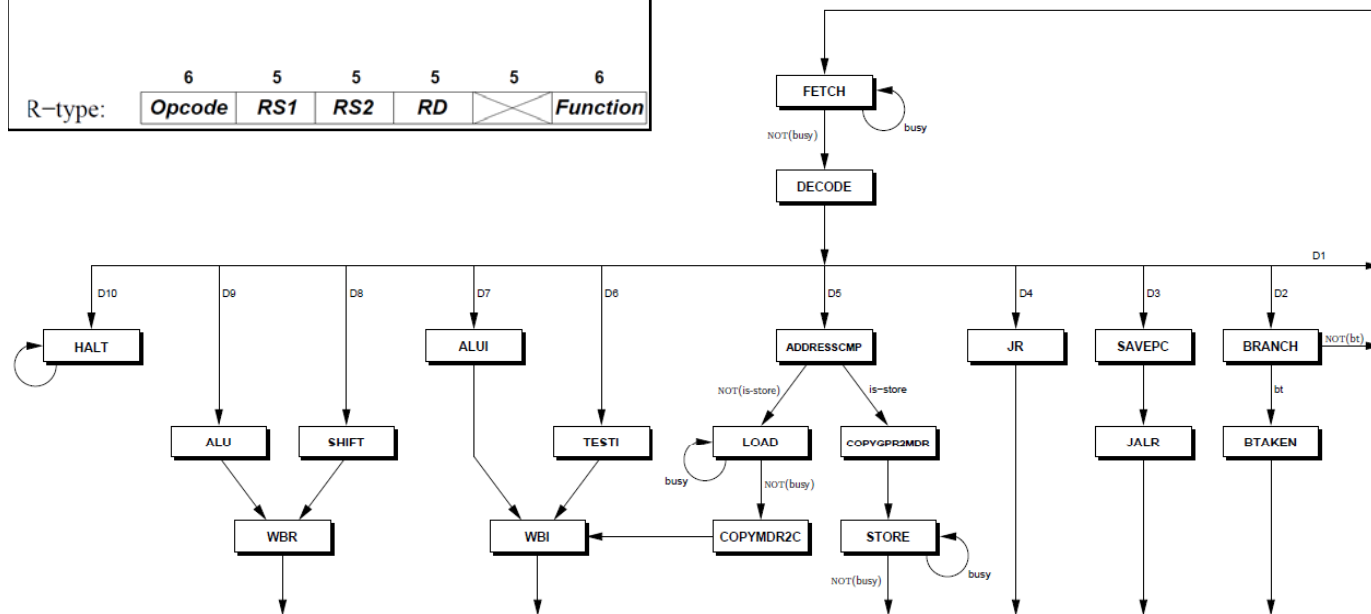 

Executing Instructions - add

Instruction	Semantics
add RD RS1 RS2	$RD := RS1 + RS2$

 

$type[4:2]$	$type[1]$	$type[0]$	$f_{type}(\vec{x}, \vec{y})$
001	1	0	$[\vec{x}] > [\vec{y}]$
010	0	0	$[\vec{x}] - [\vec{y}] \pmod{2^{32}}$
010	1	0	$[\vec{x}] = [\vec{y}]$
011	0	0	$[\vec{x}] + [\vec{y}] \pmod{2^{32}}$
011	1	0	$[\vec{x}] \geq [\vec{y}]$
100	0	0	$XOR(\vec{x}, \vec{y})$
100	1	0	$[\vec{x}] < [\vec{y}]$
101	0	0	$OR(\vec{x}, \vec{y})$
101	1	0	$[\vec{x}] \neq [\vec{y}]$
110	0	0	$AND(\vec{x}, \vec{y})$
110	1	0	$[\vec{x}] \leq [\vec{y}]$
***	*	1	$[\vec{x}] + [\vec{y}] \pmod{2^{32}}$

IR[5:0]	Mnemonic	Semantics
100 011	add	$RD = RS1 + RS2$


Executing Instructions – beqz, jalr

Instruction	Semantics
beqz RS1 imm	PC = PC + 1 + sext(imm), if RS1 = 0 PC = PC + 1, if RS1 ≠ 0
bnez RS1 imm	PC = PC + 1, if RS1 = 0 PC = PC + 1 + sext(imm), if RS1 ≠ 0
jr RS1	PC = RS1
jalr RS1	R31 = PC+1; PC = RS1

000	100
000	101


Inst[26]

beqz
bnez

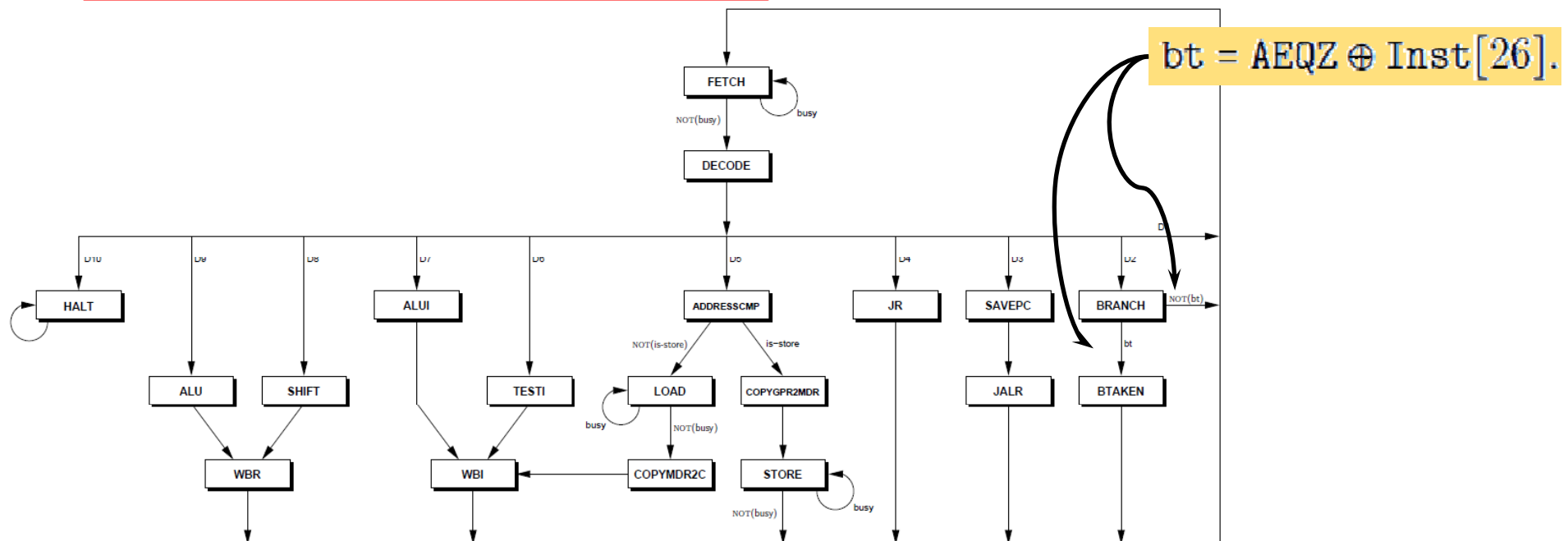

Executing Instructions - slti

Instruction	Semantics
<i>srel</i> i RD RS1 imm	RD := 1, if condition is satisfied, RD := 0 otherwise
if <i>rel</i> = 1t	test if RS1 < sext(imm)

 

$type[4:2]$	$type[1]$	$type[0]$	$f_{type}(\vec{x}, \vec{y})$
001	1	0	$[\vec{x}] > [\vec{y}]$
010	0	0	$[\vec{x}] - [\vec{y}] \pmod{2^{32}}$
010	1	0	$[\vec{x}] = [\vec{y}]$
011	0	0	$[\vec{x}] + [\vec{y}] \pmod{2^{32}}$
011	1	0	$[\vec{x}] \geq [\vec{y}]$
100	0	0	XOR(\vec{x}, \vec{y})
100	1	0	$[\vec{x}] < [\vec{y}]$
101	0	0	OR(\vec{x}, \vec{y})
101	1	0	$[\vec{x}] \neq [\vec{y}]$
110	0	0	AND(\vec{x}, \vec{y})
110	1	0	$[\vec{x}] \leq [\vec{y}]$
***	*	1	$[\vec{x}] + [\vec{y}] \pmod{2^{32}}$

IR[31:26]	Mnemonic	Semantics
011 100	slti	RD = (RS1 < sext(imm))

Executing Instructions - sw

Load/Store	Semantics
lw RD RS1 imm	$RD := M[\text{sext}(\text{imm}) + RS1]$
sw RD RS1 imm	$M[\text{sext}(\text{imm}) + RS1] := RD$

“Upgrading” the DLX – Example 1

ברצוננו להוסיף לשפת המכונה של ה – Simplified DLX
פקודת I-type חדשה:

`Chkbit17 RS1 RD`

פקודה זו גורמת לעידכון RD באופן הבא:

$$RD = \begin{cases} 0^{31} \cdot 1 & \text{if } RS1[17] = 1 \\ 0^{32} & \text{otherwise} \end{cases}$$

הציעו מימוש של ה-DLX שתומך בפקודה החדשה תוך ביצוע שינויים קטנים ככל האפשר במסלול הנתונים (הניקוד יופחת עבוק שינויים מוגזמים).

1. מנו את השינויים הנדרשים במסלול הנתונים על מנת לתמוך בהרצת הפקודה החדשה.

2. הציעו הרחבה לדיאגרמת המצבים של הבקרה על מנת לתמוך בהרצת הפקודה החדשה. ציירו את מסלול מצבי הבקרה, שמכונת המצבים חולפת דרכו בעת הרצת הפקודה החדשה. לכל מצב לאורך מסלול זה (חדש וישן), תארו את פקודת ה-RTL, שמתבצעת בו.

4.1) נוסף (מסומן באדום):


- mux

- Zero Padding - משרשר

31 אפסים משמאל.

- נמשוך את הביט ה 17


מרגיסטר A.

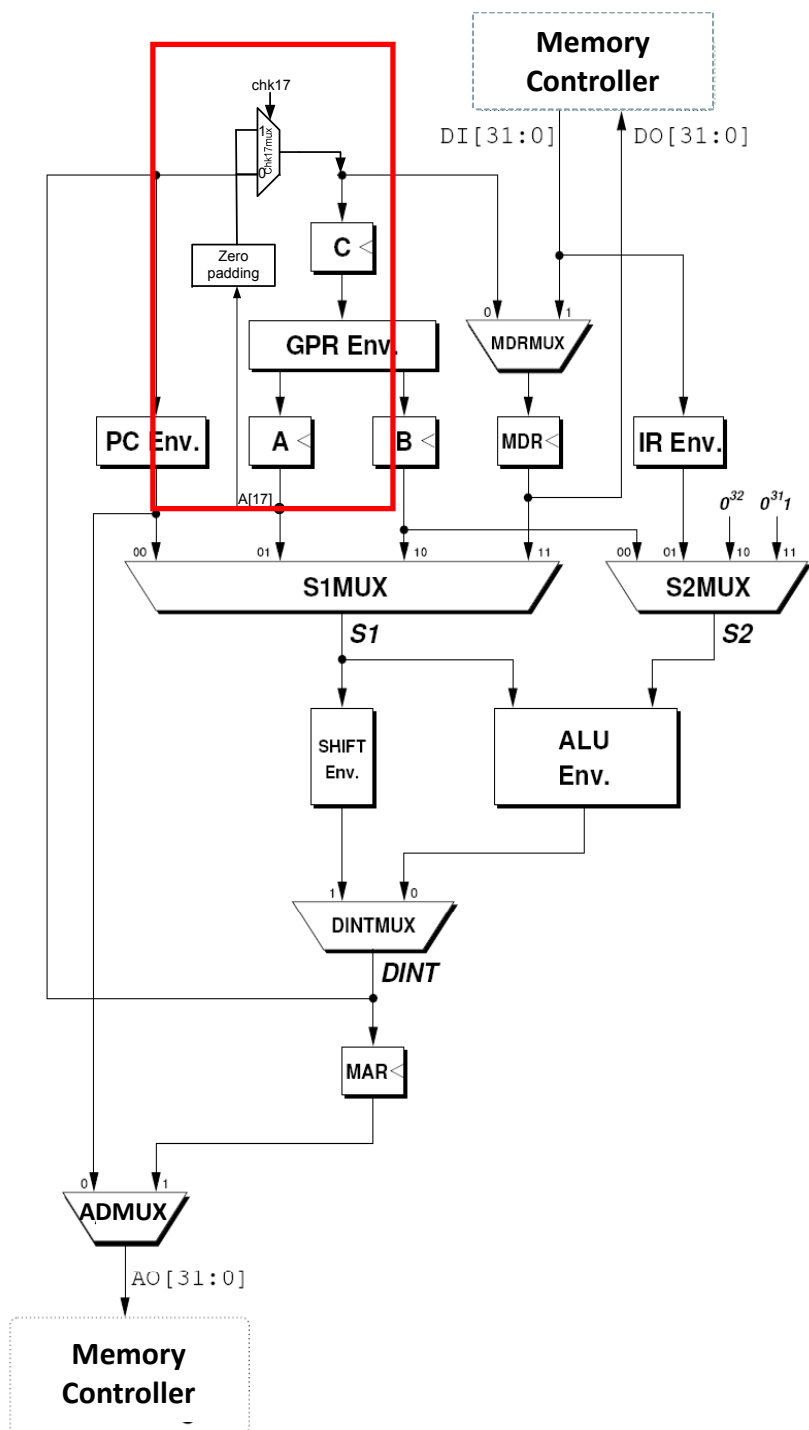

4.2) נוסף מצב נוסף – CHK17.

מסלול ביצוע הפקודה מסומן בכחול.

If OP_{CODE} = OP_{CODE}(ch_{kbit17})

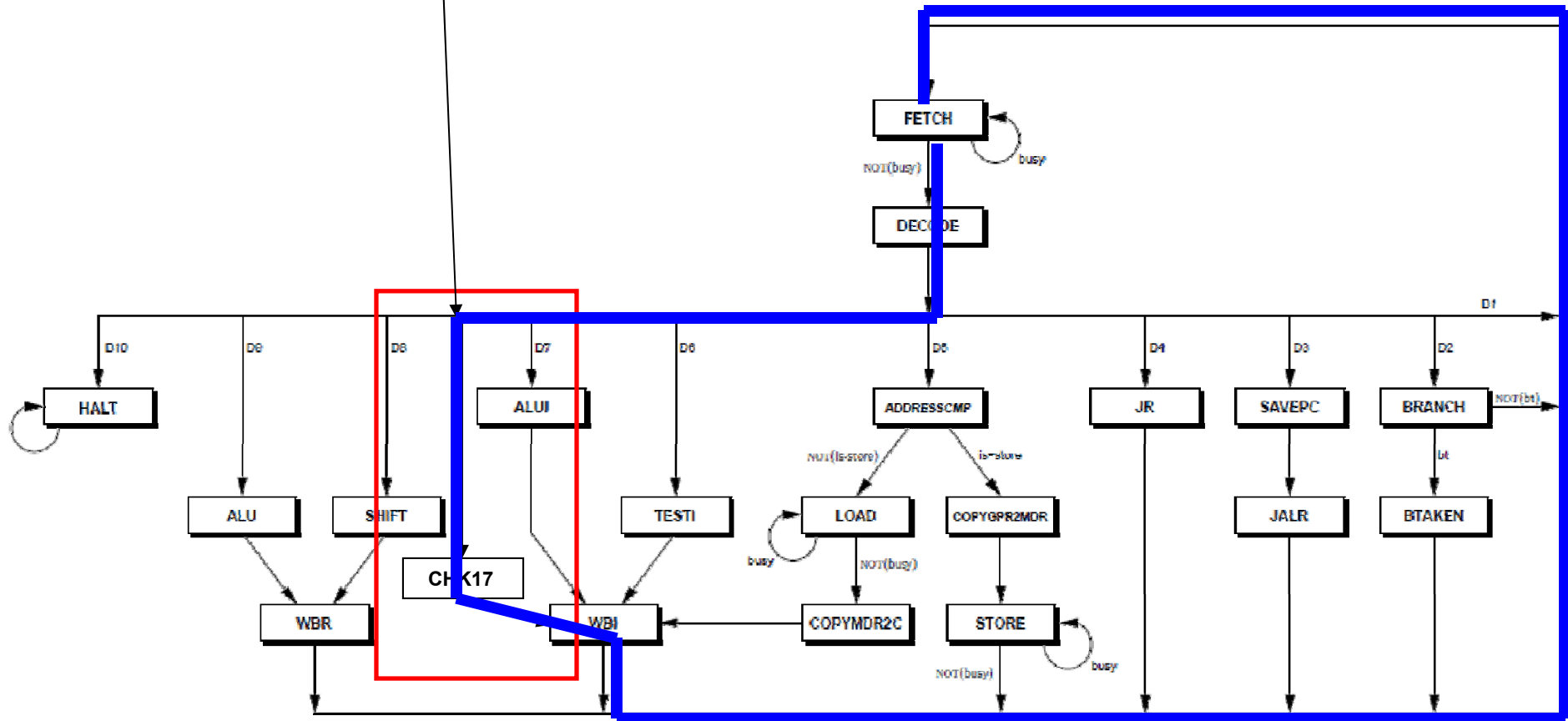

Name	RTL Instruction	Active Control Outputs
Fetch	$IR = M[PC]$	MR, IRce
Decode	$A = RS1,$ $B = RS2$ $PC = PC + 1$	Ace, Bce, S2sel[1], S2sel[0], add, PCce
Alu	$C = A \text{ op } B$	S1sel[0], Cce, active bits in ALUF[2:0]
TestI	$C = (A \text{ rel } imm)$	S1sel[0], S2sel[0], Cce, test, Itype, active bits in ALUF[2:0]
AluI(add)	$C = A + imm$	S1sel[0], S2sel[0], Cce, add, Itype
Shift	$C = A \text{ shift } sa$ $sa = 1, (-1)$	S1sel[0], Cce DINTsel, shift (,right)
Adr.Comp	$MAR = A + imm$	S1sel[0], S2sel[0], MARce, add
Load	$MDR = M[MAR]$	MDRce, ADsel, MR, MDRsel
Store	$M[MAR] = MDR$	ADsel, MW
CopyMDR2C	$C = MDR(\gg 0)$	S1sel[0], S1sel[1], S2sel[1], DINTsel, Cce
CopyGPR2MDR	$MDR = B(\ll 0)$	S1sel[1], S2sel[1], DINTsel, MDRce
WBR	$RD = C$ (R-type)	GPR_WE
WBI	$RD = C$ (I-type)	GPR_WE, Itype
Branch	branch taken?	
Btaken	$PC = PC + imm$	S2sel[0], add, PCce
JR	$PC = A$	S1sel[0], S2sel[1], add, PCce
Save PC	$C = PC$	S2sel[1], add, Cce
JALR	$PC = A$ $R31 = C$	S1sel[0], S2sel[1], add, PCce, GPR_WE, jlink
CHK17	$C = 0^{31} \cdot A[17]$	Chk17,Cce

4.2 שימו לב

שרשומים אותות

הבקרה הפעילים,

כך שאין פגיעה/שינוי

במצבים אחרים.

נוסיף את מצב

CHK17 (בכחול)

ונסיים.

``Upgrading the DLX'' – Example 2

We would like to add the following R-Type instruction:

swap *RS1* *RS2*


Semantics:

Swap between the contents of *RS1* and *RS2*.

Advised stage:

One should consider the instruction coding.


In this case: *swap RS1 RS2*

 

Changes to be made to the Data-Path and the Control's FSM:

There is no need to change the Data-Path.

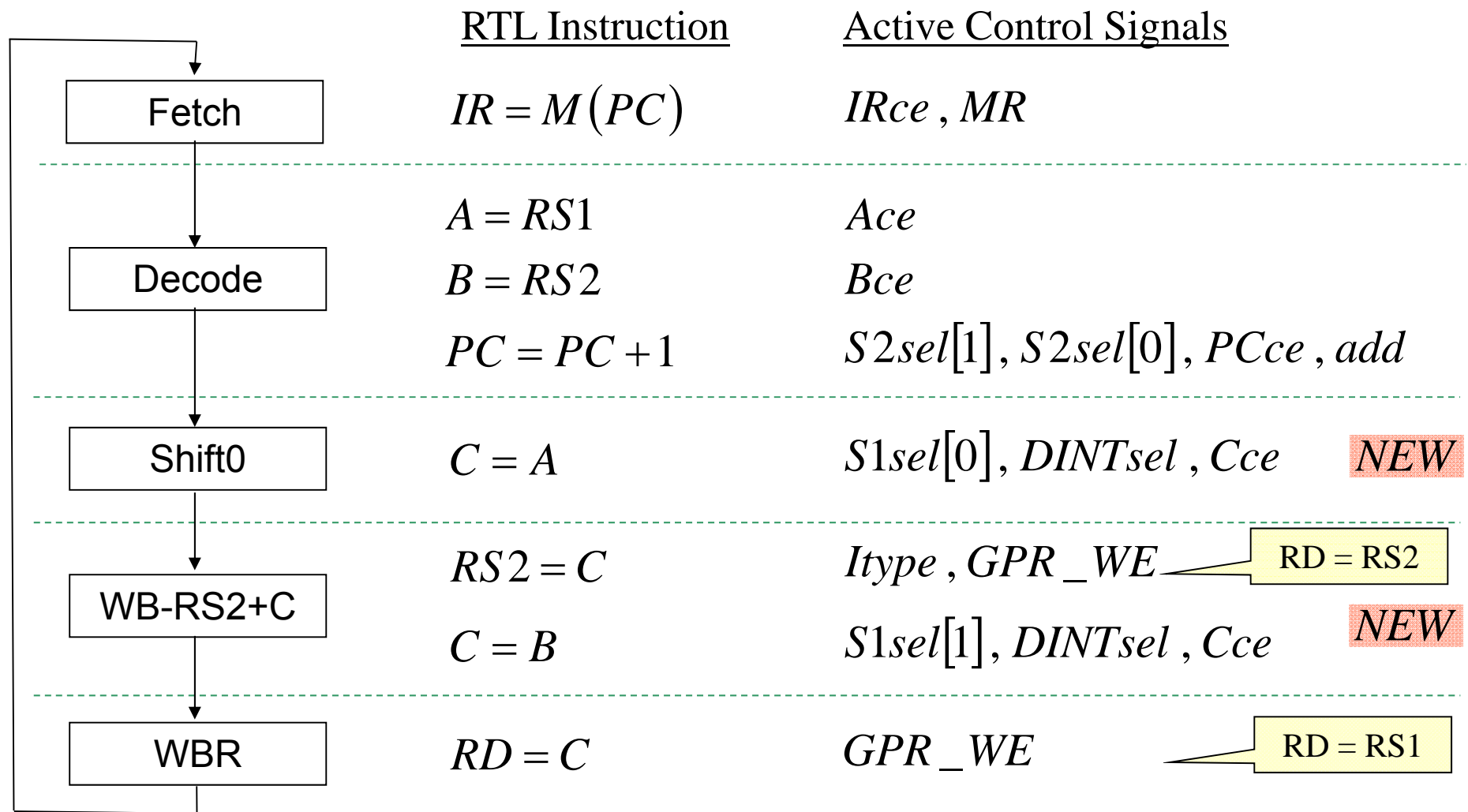Control Changes & RTL instructions of each state in the instruction execution traversal.



בהצלחה!!!